

VG-01.

$$\text{II. } I_{DA1} = -I_{D2} = -1 \text{ mA.}$$

$$I_{DA2} = I_{D1} - I_{D2} = +1 \text{ mA.}$$

Annahme in ~~Abschmitt~~ Berechnung.
Abschmitt.

für T₁: P_{沟道}.

~~U_{AS} < U_{th}~~

$$U_{AS} \leq U_{AS(th)}$$

$$U_{DD} > U_{AS(th)}, U_{DS} < 0.$$

$$I_{DA1} = -\frac{\beta}{2}(U_{AS} - U_{th})^2.$$

$$U_{th} = U_{th,0,p} + -\sqrt{(\sqrt{\phi} + U_{BSA1} - \sqrt{\phi})}$$

$$\text{未知 } U_{BSA1} = U_{DD} - U_e + U_{AS1}$$

从图中得知 U_{AS}. 查看是否符合假设.

$$\Rightarrow -\frac{2I_{DA1}}{\beta} = (U_{AS} - U_{th})^2.$$

$$U_{AS} - U_{th} = \pm \sqrt{\frac{2I_{DA1}}{\beta}}$$

$$U_{AS} = \pm \sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,0} - \sqrt{(\sqrt{\phi} + U_{DD} - U_e + U_{AS1} - \sqrt{\phi})}$$

$$U_{AS1} = \pm \sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,0} - \sqrt{(\sqrt{\phi} + U_{DD} - U_e + U_{AS1} - \sqrt{\phi})}$$

$$-\sqrt{\phi + U_{DD} - U_e + U_{AS1}} = -U_{AS1} - \underbrace{\sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,0} + \sqrt{\phi}}_{\approx U_1}. \quad \leftarrow [-(U_{AS1} - U_1)]$$

$$T^2(\phi + U_{DD} - U_e + U_{AS1}) = U_{AS1}^2 + 2U_{AS1} \cdot U_1 + U_1^2.$$

$$U_{AS1}^2 + (2U_1 + T^2)U_{AS1} + (U_1^2 - T^2U_{DD} + T^2U_e - T^2\phi) = 0$$

$$\frac{2U_1 + T^2}{2} \pm \frac{1}{2} \cdot \sqrt{(2U_1 + T^2)^2 - 4(U_1^2 - T^2U_{DD} + T^2U_e - T^2\phi)}$$

$$\text{首先 } \mp U_1, \quad U_1 = -\sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,0} + \sqrt{\phi}. \quad \approx -0.66 \text{ V}$$

$$-0.535 \text{ V} \pm 0.866 \text{ V.} \quad \text{由于 } U_{AS1} \approx -0.6. \Rightarrow U_{AS1} = -1.4 \text{ V}$$

für T₂.

$$U_{AS2} = \sqrt{\frac{2I_{DA2}}{\beta}} + U_{th,0}. \quad \Rightarrow U_{AS2} = 1.6 \text{ V} > 0.6 \text{ V.} \quad \text{nicht gesperrt}$$

$$U_{th} = U_{th,0} \Rightarrow U_{BS} = 0.$$

$$U_{DS1} = U_{D1} - U_{S1} = U_{AS2} - (U_e - U_{AS1}) = -1.4 - 2 - 1.4 = -1.801 \text{ V} \leq 0 \text{ V.}$$

$$U_{DS2} = U_{S1} = U_e - U_{AS1} = 3.4 \text{ V.} \quad \geq 0 \text{ V.}$$

符合经验. IT₂ Klar.

$$T_1: \quad U_{DD} > U_{th} \Rightarrow U_{DS} < U_{AS} - U_{th}, p \quad \checkmark$$

$$I_{P6} = I_{D2} = I_{D3}.$$

$$I_{D4} = -I_{D1} = I_{P3}.$$

$$\rightarrow \text{通过 } U_{S4} + I_{D2} \cdot R_B + U_{AS1} = U_{DD}.$$

$$U_{AS1} = U_{AS2} = \sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,n}.$$

$$= 1.047 \text{ V.}$$

$$U_{AS4} = U_{AS3} = \frac{-I_{D1}}{\beta} + U_{th,p}$$

$$= -1.047 \text{ V.}$$

$$R_B = \frac{U_{DD} + U_{AS4} - U_{AS1}}{I_{D2}}$$

$$= \frac{+2.047}{1 \text{ mA}} = 2.047 \text{ k}\Omega$$

$$M = \frac{I_{D1}}{I_{D2}} = 6.$$

由于 U_{AS} < U_{th}, 该区称为“-”

$$U_{AS} = \pm \sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,0} - \sqrt{(\sqrt{\phi} + U_{BSA1} - \sqrt{\phi})}$$

$$U_{AS1} = \pm \sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,0} - \sqrt{(\sqrt{\phi} + U_{DD} - U_e + U_{AS1} - \sqrt{\phi})}$$

$$-\sqrt{\phi + U_{DD} - U_e + U_{AS1}} = -U_{AS1} - \underbrace{\sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,0} + \sqrt{\phi}}_{\approx U_1}. \quad \leftarrow [-(U_{AS1} - U_1)]$$

$$T^2(\phi + U_{DD} - U_e + U_{AS1}) = U_{AS1}^2 + 2U_{AS1} \cdot U_1 + U_1^2.$$

$$U_{AS1}^2 + (2U_1 + T^2)U_{AS1} + (U_1^2 - T^2U_{DD} + T^2U_e - T^2\phi) = 0$$

$$\frac{2U_1 + T^2}{2} \pm \frac{1}{2} \cdot \sqrt{(2U_1 + T^2)^2 - 4(U_1^2 - T^2U_{DD} + T^2U_e - T^2\phi)}$$

$$\text{首先 } \mp U_1, \quad U_1 = -\sqrt{\frac{2I_{DA1}}{\beta}} + U_{th,0} + \sqrt{\phi}. \quad \approx -0.66 \text{ V}$$

$$-0.535 \text{ V} \pm 0.866 \text{ V.} \quad \text{由于 } U_{AS1} \approx -0.6. \Rightarrow U_{AS1} = -1.4 \text{ V}$$

für T₂.

$$U_{AS2} = \sqrt{\frac{2I_{DA2}}{\beta}} + U_{th,0}. \quad \Rightarrow U_{AS2} = 1.6 \text{ V} > 0.6 \text{ V.} \quad \text{nicht gesperrt}$$


$$U_{th} = U_{th,0} \Rightarrow U_{BS} = 0.$$

$$U_{DS1} = U_{D1} - U_{S1} = U_{AS2} - (U_e - U_{AS1}) = -1.4 - 2 - 1.4 = -1.801 \text{ V} \leq 0 \text{ V.}$$

$$U_{DS2} = U_{S1} = U_e - U_{AS1} = 3.4 \text{ V.} \quad \geq 0 \text{ V.}$$

符合经验. IT₂ Klar.

(z1) Kleinsignal - Ersatzschaltung.

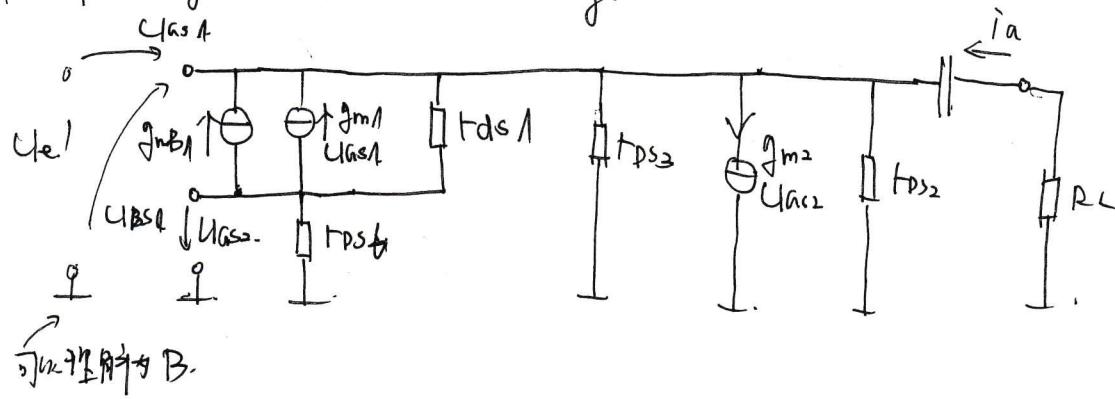

$$g_{m1} = \sqrt{-2\beta \cdot I_{PA} \cdot (1 - \alpha U_{PA1})} \approx \sqrt{-2\beta \cdot I_{DA}} = 4.47 \text{ mS}$$

$$g_{mB1} = \frac{r \cdot g_n}{2\sqrt{\phi - U_{DS1}}} = 0.77 \text{ mS}$$

$$g_{m2} = \sqrt{2 \cdot \beta \cdot I_{PA2}} = 10 \text{ mS}$$

$$t_{DS1} = \frac{V_s - U_{DS1}}{-I_{PA1}} \approx -\frac{1}{\lambda I_{PA1}} = 40 \text{ k}\Omega$$

$$t_{DS1} = t_{DS2} = 40 \text{ k}\Omega \quad t_{DS3} \text{ ist } \neq \text{ fest}$$

zu 3. Aufgabe B.

$$t_a = \left. \frac{U_a'}{I_a} \right|_{U_a' = 0}$$

$$\textcircled{1} \quad i_a' = \frac{U_a'}{t_{DS2}} + \frac{U_a'}{t_{DS3}} + g_m U_{GS2} + U_{GS2}/t_{DS6}$$

$$\textcircled{2} \quad U_e' \text{ ist } 0, \quad U_e' = 0, \quad \rightarrow U_{GS1} = U_{DS1} = -U_a'$$

$$\textcircled{3} \quad U_a' = g_m \cdot i_a' \cdot (g_{m1} + g_{mB1}) \cdot t_{DS1} = U_{GS1} \cdot U_{GS2},$$

$$U_{GS2} + \left[(g_{mB1} + g_m)(U_a') + \frac{U_{GS2}}{t_{DS4}} \right] \cdot t_{DS1} \Rightarrow \text{Punkt } g_m U_a'$$

$\cancel{U_a'}$	$U_{GS2} + U_{GS2} \cdot \frac{t_{DS1}}{t_{DS4}} + t_{DS1} \cdot i_a' (g_{mB1} + g_m) = U_a'$
$\cancel{i_a'}$	$U_a' = \frac{U_{GS2} + U_{GS2} \left(\frac{t_{DS1}}{t_{DS4}} \right)}{1 + t_{DS1}(g_{mB1} + g_m)}$

$$g_{FB} = \frac{1}{F} = \frac{I_a}{U_a} = \frac{1}{t_{DS2}} + \frac{1}{t_{DS3}} + \frac{g_m U_{GS2} [1 - t_{DS1}(g_{mB1} + g_m)]}{U_{GS2} [1 + \frac{t_{DS1}}{t_{DS6}}]} + \frac{[1 + t_{DS1}(g_{mB1} + g_m)]}{t_{DS6} [1 + \frac{t_{DS1}}{t_{DS6}}]}$$

$\cancel{t_{DS2}}, \cancel{t_{DS3}}$

$$F = \frac{1}{\frac{1}{t_{DS2}} + \frac{1}{t_{DS3}} + \frac{g_m}{2} [1 - t_{DS1}(g_{mB1} + g_m) + \frac{[1 + t_{DS1}(g_{mB1} + g_m)]}{2 t_{DS6}}]}$$

$$T_{a'} = \frac{\frac{1}{T_{DS2}} + \frac{1}{T_{DS3}} + \left(g_{m2} + \frac{1}{T_{DS6}}\right) \cdot \frac{1}{1 + T_{DS1}(g_{m1} + g_m)}}{g_{m2}(1 + T_{DS1}(g_{m1} + g_m))}$$

$$A_{\lambda} \cdot T_{a'} = \frac{\frac{2}{g_{m2} T_{DS1}(g_{m1} + g_m)}}{ms \text{ kV ms}} = f. 542 \quad [kV] \approx 0.954 \text{ kV}$$

Verstärkung,

$$V' = \frac{U_{a'}}{U_{be}}$$

$$(1) U_{BS1} = -U_{a'} \quad U_{AS1} = U_{e'} - U_{a'}$$

$$\left[\frac{U_{a'} - U_{AS2}}{T_{DS1}} + g_{mB1} \cdot U_{a'} - g_{m1}(U_{e'} - U_{a'}) \right] \cancel{+ T_{DS1} \cdot T_{DS6}} = U_{AS2}$$

$$\cancel{U_{a'} - U_{AS2} + T_{DS6} \cdot g_{mB1} \cdot U_{a'} - T_{DS6} \cdot g_{m1} U_{e'} + g_{m1} U_{a'}} = U_{AS2}$$

$$U_{a'} + T_{DS6}(g_{mB1} + g_{m1}) U_{a'} - T_{DS6} g_{m1} U_{e'} = 2U_{AS2}, \quad (1)$$

$$\frac{U_{AS2}}{T_{DS6}} \neq \frac{U_{a'}}{R_L} + \frac{U_{a'}}{T_{DS2}} + \frac{U_{a'}}{R_{DS3}} + g_{m2} U_{AS2} = 0 \quad (2)$$

$$\Rightarrow U_{AS2} = \frac{-\left[\frac{U_{a'}}{R_L} + \frac{U_{a'}}{T_{DS2}} + \frac{U_{a'}}{R_{DS3}}\right]}{\frac{1}{T_{DS6}} + g_{m2}}$$

$$T_{DS6} g_{m1}$$

$$T_{DS6}(g_{mB1} + g_{m1}) + \frac{2\left[\frac{1}{R_L} + \frac{1}{T_{DS2}} + \frac{1}{R_{DS3}}\right]}{\frac{1}{T_{DS6}} + g_{m2}} = V' \quad \rightarrow 0.84$$

Max 3-fach Verstärkung mit R_L

V_{G-D^2}

Vortlesung CTA

$$U_{DS} + U_{GS} = U_{TH} \rightarrow U_{GS} = U_{TH}$$


$$U_a = U_{DS2} + U_{DS4}; \quad U_{DS2, \text{sat}} = U_{GS} - U_{TH} = \sqrt{\frac{2I_a}{\rho}}$$

$$U_{DS2} = -U_{GS4} + U_{GS3} + U_{GS1} = -U_{GS4} + U_{GS3} + U_{GS2}.$$

$$U_{GS3} = U_{GS4} \Rightarrow U_{DS2} = U_{GS2}.$$

这里互补对太麻烦 - 先用图解

要让两个管子都工作在饱和区

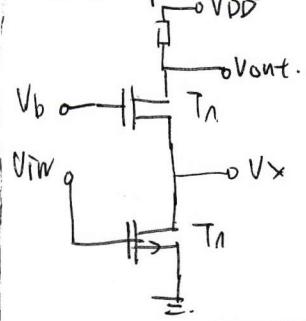

$$\text{对于 } Tn_1: V_x > V_{in} - V_{th1}, \quad V_x = V_b - V_{GS2} \Rightarrow V_b > V_{in} - V_{th1} + U_{GS2}.$$

$$V_{out} > V_b - V_{th2} \Rightarrow V_{out} > V_{th2} - V_{th1} + U_{GS2} - U_{th1}.$$

$$\text{在用TAS方法时有 } U_{GS2} = \Delta U_{D4} / [I_{GS3} + g_m b_3] \approx 0.3V$$

$$\text{对于 } Tn_2: U_{DS1} = U_{DS2} \Rightarrow V_{out} \text{ 由 } V_{out} = I_D3 = I_{D4} \Rightarrow U_{GS3} = U_{GS4}$$

$$U_{DS4, \text{min}} = U_{DS4, \text{sat}} = \sqrt{\frac{2I_a}{\rho}} = 0.316V$$

$$U_{a, \text{min}} = U_{DS2} + U_{DS4} \Big|_{min} = U_{GS2} + U_{DS4, \text{min}} = U_{DS2, \text{sat}} + U_{th1} + U_{DS4, \text{min}}$$

$$= \sqrt{\frac{8I_a}{\rho}} = 1.23V. \quad U_{GS2} (U_{th1}) + U_{th1} = 1.23V.$$

$$U_{DS1} \geq U_{GS1} - U_{th}. \rightarrow U_{GS1} \leq U_{DS1} + U_{th} \leq U_{DS1} + U_{GS3}.$$

$$\Rightarrow I_{ref} = \frac{I_a}{f} \Rightarrow f = \frac{\rho}{2I_a}. \quad \text{由 } f \propto \beta \text{ 为反比例关系.}$$

$$(1) U_{a, \text{min}} = U_{DS2, \text{sat}} + U_{DS4, \text{sat}} = 2 \cdot U_{DS, \text{sat}} = 0.4V \quad U_{GS3} \neq U_{GS4}$$


$$U_{GS4} - U_{th} = U_{DS, \text{sat}} \Rightarrow U_{GS4} = U_{DS, \text{sat}} + U_{th} = 0.4 + 0.8V$$

$$U_{GS4} = U_{GS3,4} = U_{GS4} + U_{DS, \text{sat}} = 0.8 + 0.2 = 1V.$$

$$R_B = \frac{U_{GS3,4} - U_{GS4}}{I_D} = \frac{U_{DS, \text{sat}}}{I_D} = \frac{0.2}{1 \times 10^{-4}} = 2 \times 10^3 = 2k\Omega. \quad \beta = f.$$

$$R_o = \frac{U_{GS4}}{I_D} = \frac{1}{1 \times 10^{-4}} = 10^4 \Omega = 10k\Omega.$$
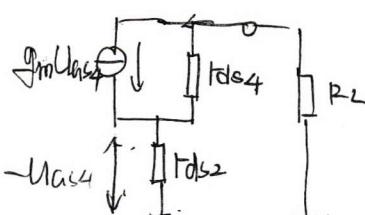
$$(2) \text{ 反相器 - 反相器串行组合} \quad U_{DS} - U_{GS3,4} / I_D = \frac{2}{1 \times 10^{-4}} = 20k\Omega. \Rightarrow R = R_o + R_B = 21k\Omega.$$



$$f_n = \frac{2I_D}{2\beta I_{DA}} = \sqrt{2 \cdot f \cdot 0.1} = 1 \text{ ms}$$

$$I_{DS} = \frac{U_A + U_{GS4}}{2I_{DA}} \approx \frac{1}{2I_{DA}} \approx 2f_0 k\Omega.$$

$$\left\{ -\frac{U_{GS4}}{I_{DS2}} = I_a. \right.$$

$$\left(-\frac{U_{GS4}}{I_{DS2}} - g_m U_{GS4} \right) I_{DS4} + U_{GS4} = I_a.$$

$$\Rightarrow -(g_m + 1) U_{GS4} = U_a \Rightarrow f_0 = I_{DS2} (g_m + 1) \approx 62.5 \text{ Hz}$$

$$(3) U_{GS}(T) = \sqrt{\frac{2I_D}{\beta}} + U_{th}$$

$$\frac{\partial U_{GS}}{\partial T} \Big|_{T=T_0} = \boxed{\frac{\partial I_D}{\partial T} \Big|_{T=T_0} + \frac{\partial U}{\partial T}}$$

$$\frac{\partial U_{GS}(T)}{\partial I_D} \Big|_{T=T_0} \cdot \frac{\partial I_D}{\partial T} \Big|_{T=T_0} +$$

$$\frac{\partial U_{GS}(T)}{\partial \beta} \Big|_{T=T_0} \cdot \frac{\partial \beta}{\partial T} \Big|_{T=T_0} +$$

$$\frac{\partial U_{GS}(T)}{\partial U_{th}} \Big|_{T=T_0} - \frac{\partial U_{th}}{\partial T} \Big|_{T=T_0} .$$

Auf. $I_0 = I_o \Rightarrow \text{konst.}$

$$\frac{\partial U_{GS}(T)}{\partial \beta} = \frac{-2I_D \cdot \frac{1}{\beta^2}}{\sqrt{\frac{2I_D}{\beta}}} \Big|_{T=T_0} = -\frac{\sqrt{2I_D}}{\beta^2 \sqrt{\frac{2}{\beta}}}$$

$$\frac{\partial \beta}{\partial T} \Big|_{T=T_0} = \frac{\beta_0}{T_0} \cdot -\frac{3}{2} \sqrt{\frac{T}{T_0}} \Big|_{T=T_0}^{-\frac{1}{2}} = -\frac{3}{2} \frac{\beta_0}{T_0}$$

$$\frac{\partial U_{GS}}{\partial U_{th}} \Big|_{T=T_0} = 1, \quad \frac{\partial U_{th}}{\partial T} \Big|_{T_0} = -1 \text{ mV/K}.$$

$$\Rightarrow -\frac{3}{2} \frac{\beta_0}{T_0} \cdot -\frac{\sqrt{2\beta I_D}}{\beta_0^2 \sqrt{\frac{2}{\beta}}} = +\frac{3}{4T_0} \sqrt{\frac{2I_D}{\beta_0}}$$

$$\cancel{\frac{\partial U_{GS}}{\partial T} \Big|_{T=T_0}} = \cancel{+\frac{3}{4T_0} \sqrt{\frac{2I_D}{\beta_0}}} - 1 \cdot \frac{mV}{K} = -0.5 \text{ mV/K}.$$

